

## Electric Circuits

An electric circuit is a *complete pathway* that allows *electrons* to flow. Electric potential is provided at a source and is "used" by elements of a completed electric circuit.

**Define each of the following basic components of an electric circuit.**

(a) source - the source of electrical energy (example: a battery)










(b) conductor - the wire through which electric current flows .

(c) load - a device that transform electrical energy into other forms of energy (example: a lightbulb)

(d) switch - a device that can turn the circuit on or off by closing or opening the circuit

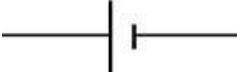
**Draw the circuit symbol for each component**

**See page 262**


Component	Circuit Symbol
1. conducting wire	
2. bulb	
3. voltmeter	
4. open switch	
5. cell	
6. closed switch	
7. battery (3 cells)	
8. ammeter	
9. resistor	

**Draw a proper circuit diagram for each of the following circuits.**


Circuit A

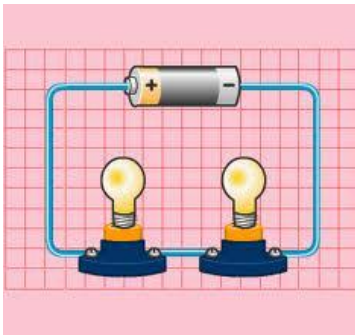


Circuit Diagram A

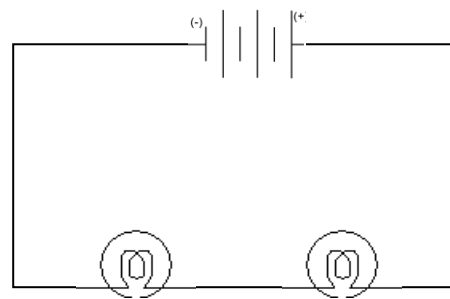


Circuit B

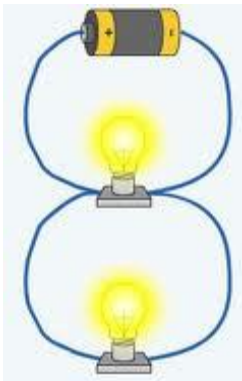


Circuit Diagram B

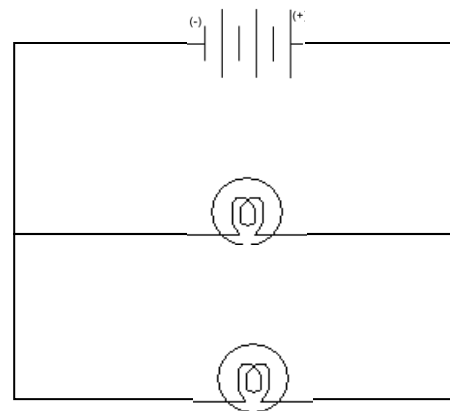

Circuit C

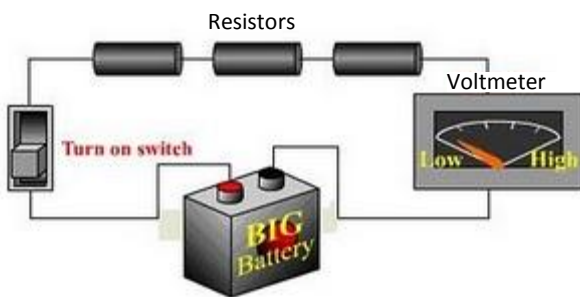

Circuit Diagram C

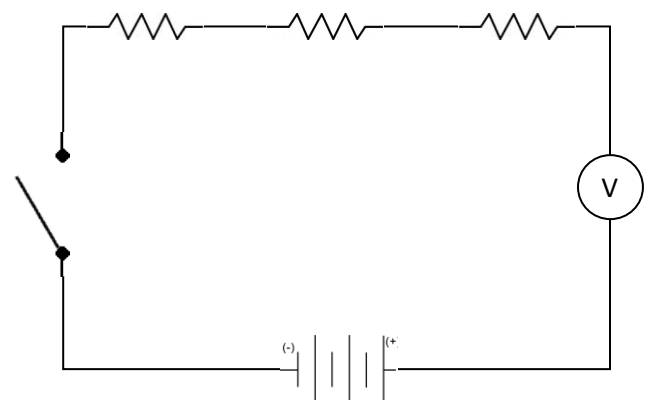

**Complete 8-2B “Drawing Circuit Diagrams” on page 263 in your notebook.**